

COM 251 Logic Design and Circuits

Combinational Logic Design: Decoders and Multiplexers

Prof. Dr. Halûk Gümüşkaya

haluk.gumuskaya@gediz.edu.tr

haluk@gumuskaya.com <http://www.gumuskaya.com>

Computer Engineering Department

GEDİZÜNİVERSİTESİ
izmir

Thursday, October 27, 2011

1

Acknowledgement

The slides have been based in-part upon original slides of a number of books including:

- *Digital Design with RTL Design, Verilog and VHDL*, 2nd ed., Frank Vahid, John Wiley, 2011.
- *Logic and Computer Design Fundamentals*, 4th Ed., M. Morris Mano, C. Kime, Prentice Hall, 2008.

2

Overview

- **Functions and functional blocks**
- **Rudimentary logic functions**
- **Decoding using Decoders**
 - **Implementing Combinational Functions with Decoders**
- **Encoding using Encoders**
- **Selecting using Multiplexers**
 - **Implementing Combinational Functions with Multiplexers**

3

Functions and Functional Blocks

- The functions considered are those found to be very useful in design
- Corresponding to each of the functions is a combinational circuit implementation called a *functional block*.
- In the past, **functional blocks** were packaged as small-scale-integrated (SSI), medium-scale integrated (MSI), and large-scale-integrated (LSI) circuits.
- Today, they are often simply implemented within a very-large-scale-integrated (VLSI) circuit.


4

Rudimentary Logic Functions

- Functions of a single variable X
- Can be used on the inputs to functional blocks to implement other than the block's intended function

TABLE 4-1
Functions of One Variable


X	F = 0	F = X	F = \bar{X}	F = 1
0	0	0	1	1
1	0	1	0	1

 

5

Multiple-bit Rudimentary Functions

Multi-bit Examples:

 


- A wide line is used to represent a bus which is a vector signal
- In (b) of the example, $F = (F_3, F_2, F_1, F_0)$ is a bus.
- The bus can be split into individual bits as shown in (b)
- Sets of bits can be split from the bus as shown in (c) for bits 2 and 1 of F.
- The sets of bits need not be continuous as shown in (d) for bits 3, 1, and 0 of F.

6

Enabling Function

 
- Enabling permits an input signal to pass through to an output
- Disabling blocks an input signal from passing through to an output, replacing it with a fixed value
- The value on the output when it is disabled can be Hi-Z (as for three-state buffers and transmission gates), 0, or 1
- When disabled, 0 output
- When disabled, 1 output
- See Enabling App in text



7

Decoders

- Decoder:** Popular combinational logic building block, in addition to logic gates
 - Converts input binary number to one high output
- 2-input decoder: four possible input binary numbers
 - So has four outputs, one for each possible input binary number
- Internal design
 - AND gate for each output to detect input combination
- Decoder with enable e
 - Outputs all 0 if $e=0$
 - Regular behavior if $e=1$
- n-input decoder: 2^n outputs

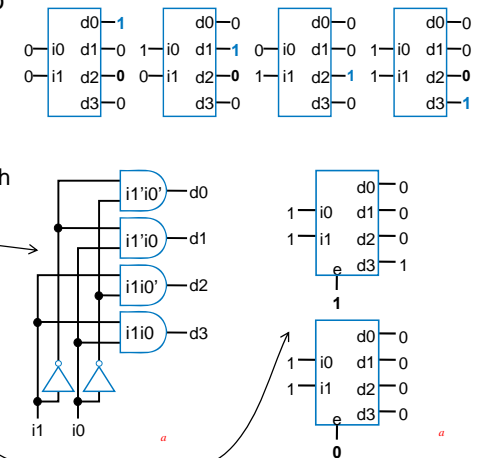


2.9

8

Decoder Example

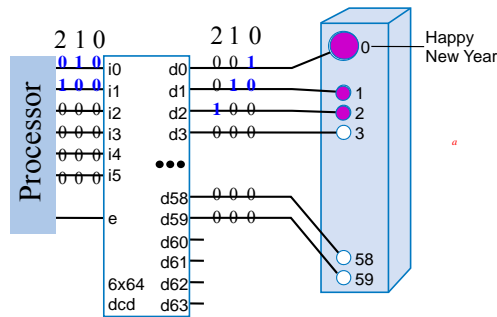- New Year's Eve Countdown Display
 - Microprocessor counts from 59 down to 0 in binary on 6-bit output
 - Want illuminate one of 60 lights for each binary number
 - Use 6x64 decoder
 - 4 outputs unused



9

Decoding


- Decoding - the conversion of an n -bit input code to an m -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- Circuits that perform decoding are called *decoders*
- Here, functional blocks for decoding are
 - called n -to- m line decoders, where $m \leq 2^n$, and
 - generate 2^n (or fewer) minterms for the n input variables

10

Decoder Examples

- 1-to-2-Line Decoder


A	D ₀	D ₁
0	1	0
1	0	1

 

- 2-to-4-Line Decoder

A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

 

(b)

- Note that the 2-4-line made up of 2 1-to-2-line decoders and 4 AND gates.

11

Decoder Expansion

- General procedure given in book for any decoder with n inputs and 2^n outputs.
- This procedure builds a decoder backward from the outputs.
- The output AND gates are driven by two decoders with their numbers of inputs either equal or differing by 1.
- These decoders are then designed using the same procedure until 2-to-1-line decoders are reached.
- The procedure can be modified to apply to decoders with the number of outputs $\neq 2^n$

12


Decoder Expansion - Example 1

- 3-to-8-line decoder
 - Number of output ANDs = 8
 - Number of inputs to decoders driving output ANDs = 3
 - Closest possible split to equal
 - 2-to-4-line decoder
 - 1-to-2-line decoder
 - 2-to-4-line decoder
 - Number of output ANDs = 4
 - Number of inputs to decoders driving output ANDs = 2
 - Closest possible split to equal
 - Two 1-to-2-line decoders
- See next slide for result

13

Decoder Expansion - Example 1

Result

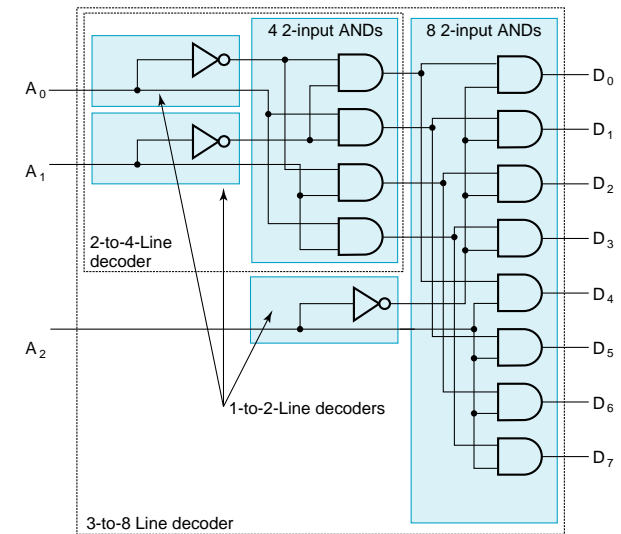

14

Decoder Expansion - Example 2

- 7-to-128-line decoder
 - Number of output ANDs = 128
 - Number of inputs to decoders driving output ANDs = 7
 - Closest possible split to equal
 - 4-to-16-line decoder
 - 3-to-8-line decoder
 - 4-to-16-line decoder
 - Number of output ANDs = 16
 - Number of inputs to decoders driving output ANDs = 2
 - Closest possible split to equal
 - 2 2-to-4-line decoders
 - Complete using known 3-8 and 2-to-4 line decoders


15

Decoder with Enable

- In general, attach m -enabling circuits to the outputs
- See truth table below for function
 - Note use of X's to denote both 0 and 1
 - Combination containing two X's represent four binary combinations
- Alternatively, can be viewed as distributing value of signal EN to 1 of 4 outputs
- In this case, called a *demultiplexer*

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

(a)

 

(b)

16

Combinational Logic Implementation - Decoder and OR Gates

- Implement m functions of n variables with:
 - Sum-of-minterms expressions
 - One n -to- 2^n -line decoder
 - m OR gates, one for each output
- Approach 1:
 - Find the truth table for the functions
 - Make a connection to the corresponding OR from the corresponding decoder output wherever a 1 appears in the truth table
- Approach 2
 - Find the minterms for each output function
 - OR the minterms together

17

Decoder and OR Gates Example

- Implement the following set of odd parity functions of (A_7, A_6, A_5, A_3)

$$P_1 = A_7 \oplus A_5 \oplus A_3$$

$$P_2 = A_7 \oplus A_6 \oplus A_3$$

$$P_4 = A_7 \oplus A_6 \oplus A_5$$


- Finding sum of minterms expressions

$$P_1 = \sum_m(1,2,5,6,8,11,12,15)$$

$$P_2 = \sum_m(1,3,4,6,8,10,13,15)$$

$$P_4 = \sum_m(2,3,4,5,8,9,14,15)$$

- Find circuit
- Is this a good idea?

 

18

Encoding

- Encoding - the opposite of decoding - the conversion of an m -bit input code to a n -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- Circuits that perform encoding are called *encoders*
- An encoder has 2^n (or fewer) input lines and n output lines which generate the binary code corresponding to the input values
- Typically, an encoder converts a code containing exactly one bit that is 1 to a binary code corresponding to the position in which the 1 appears.

19

Encoder Example

- A decimal-to-BCD encoder
 - Inputs: 10 bits corresponding to decimal digits 0 through 9, (D_9, \dots, D_0)
 - Outputs: 4 bits with BCD codes
 - Function: If input bit D_i is a 1, then the output (A_3, A_2, A_1, A_0) is the BCD code for i ,
- The truth table could be formed, but alternatively, the equations for each of the four outputs can be obtained directly.

20

Encoder Example (continued)

- Input D_i is a term in equation A_j if bit A_j is 1 in the binary value for i .
- Equations:

$$A_3 = D_8 + D_9$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_0 = D_1 + D_3 + D_5 + D_7 + D_9$$
- $F_1 = D_6 + D_7$ can be extracted from A_2 and A_1 . Is there any cost saving?

21

Priority Encoder

- If more than one input value is 1, then the encoder just designed does not work.
- One encoder that can accept all possible combinations of input values and produce a meaningful result is a *priority encoder*.
- Among the 1s that appear, it selects the most significant input position (or the least significant input position) containing a 1 and responds with the corresponding binary code for that position.

22

Priority Encoder Example

- Priority encoder with 5 inputs (D_4, D_3, D_2, D_1, D_0) - highest priority to most significant 1 present - Code outputs A_2, A_1, A_0 and V where V indicates at least one 1 present.

No. of Min-terms/Row	Inputs					Outputs			
	D4	D3	D2	D1	D0	A2	A1	A0	V
1	0	0	0	0	0	X	X	X	0
1	0	0	0	0	1	0	0	0	1
2	0	0	0	1	X	0	0	1	1
4	0	0	1	X	X	0	1	0	1
8	0	1	X	X	X	0	1	1	1
16	1	X	X	X	X	1	0	0	1

- Xs in input part of table represent 0 or 1; thus table entries correspond to product terms instead of minterms. The column on the left shows that all 32 minterms are present in the product terms in the table

23

Priority Encoder Example (continued)

- Could use a K-map to get equations, but can be read directly from table and manually optimized if careful:

$$A_2 = D_4$$

$$A_1 = \bar{D}_4 D_3 + \bar{D}_4 \bar{D}_3 D_2 = \bar{D}_4 F_1, \quad F_1 = (D_3 + D_2)$$


$$A_0 = \bar{D}_4 D_3 + \bar{D}_4 \bar{D}_3 \bar{D}_2 D_1 = \bar{D}_4 (D_3 + \bar{D}_2 D_1)$$

$$V = D_4 + F_1 + D_1 + D_0$$

24

Multiplexor (Mux)

 - Mux: Another popular combinational building block
 - Routes one of its N data inputs to its one output, based on binary value of select inputs
 - 4 input mux → needs 2 select inputs to indicate which input to route through
 - 8 input mux → 3 select inputs
 - N inputs → $\log_2(N)$ selects
 - Like a rail yard switch



25

Selecting: Multiplexers

- Selecting of data or information is a critical function in digital systems and computers
- Circuits that perform selecting have:
 - A set of information inputs from which the selection is made
 - A single output
 - A set of control lines for making the selection
- Logic circuits that perform selecting are called *multiplexers*
- Selecting can also be done by three-state logic or transmission gates


26

Multiplexers

- A multiplexer selects information from an input line and directs the information to an output line
- A typical multiplexer has n control inputs (S_{n-1}, \dots, S_0) called *selection inputs*, 2^n information inputs (I_{2^n-1}, \dots, I_0), and one output Y
- A multiplexer can be designed to have m information inputs with $m < 2^n$ as well as n selection inputs

27


Mux Internal Design

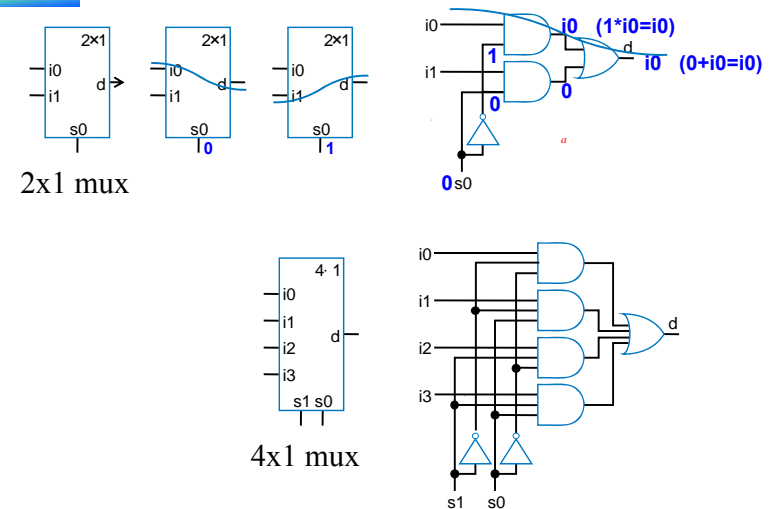

28


Mux Example

 - City mayor can set 4 switches up or down, representing his/her vote on each of four proposals, numbered 0, 1, 2, 3
- City manager can display any such vote on large green/red LED (light) by setting two switches to represent binary 0, 1, 2, or 3
- Use 4x1 mux



29


Muxes Commonly Together – N-bit Mux

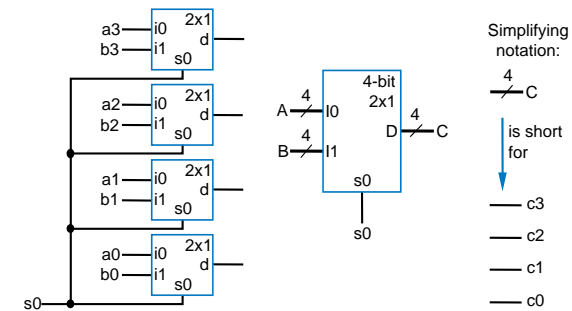

- Ex: Two 4-bit inputs, A (a3 a2 a1 a0), and B (b3 b2 b1 b0)
 - 4-bit 2x1 mux (just four 2x1 muxes sharing a select line) can select between A or B

30

N-bit Mux Example

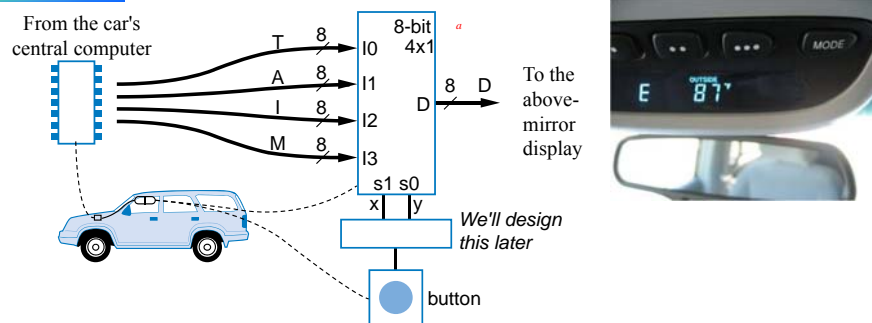

- Four possible display items
 - Temperature (T), Average miles-per-gallon (A), Instantaneous mpg (I), and Miles remaining (M) – each is 8-bits wide
 - Choose which to display on D using two inputs x and y
 - Pushing button sequences to the next item
 - Use 8-bit 4x1 mux

31


2-to-1-Line Multiplexer

- Since $2 = 2^1$, $n = 1$
- The single selection variable S has two values:
 - S = 0 selects input I_0
 - S = 1 selects input I_1

- The equation:

$$Y = \bar{S}I_0 + SI_1$$

- The circuit:

 

32


2-to-1-Line Multiplexer (continued)

- Note the regions of the multiplexer circuit shown:
 - 1-to-2-line Decoder
 - 2 Enabling circuits
 - 2-input OR gate
- To obtain a basis for multiplexer expansion, we combine the Enabling circuits and OR gate into a 2×2 AND-OR circuit:
 - 1-to-2-line decoder
 - 2×2 AND-OR
- In general, for an 2^n -to-1-line multiplexer:
 - n -to- 2^n -line decoder
 - $2^n \times 2$ AND-OR

33

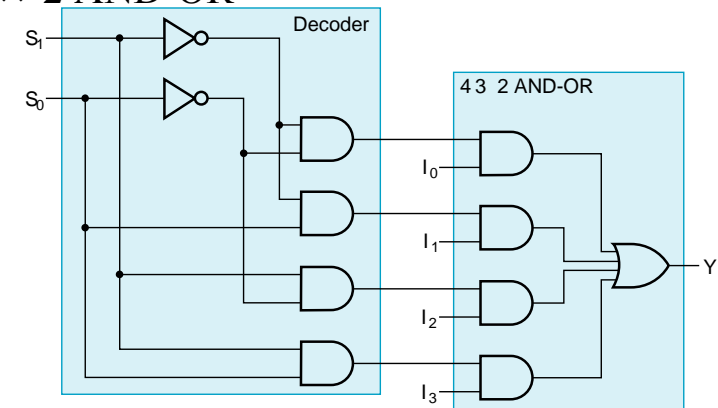Example: 4-to-1-line Multiplexer


- 2-to- 2^2 -line decoder
- $2^2 \times 2$ AND-OR



34

Multiplexer Width Expansion

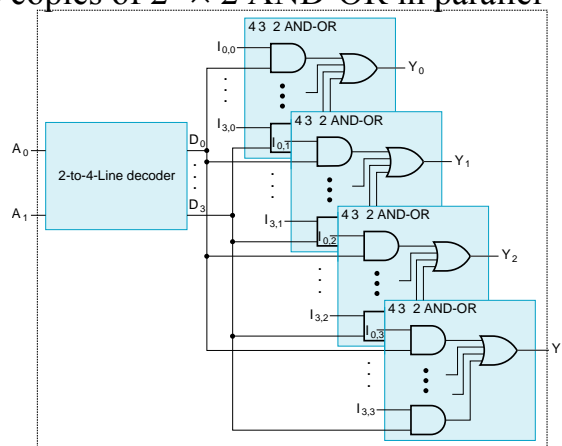
- Select “vectors of bits” instead of “bits”
- Use multiple copies of $2^n \times 2$ AND-OR in parallel
- Example: 4-to-1-line quad multiplexer



35

Other Selection Implementations

- Three-state logic in place of AND-OR

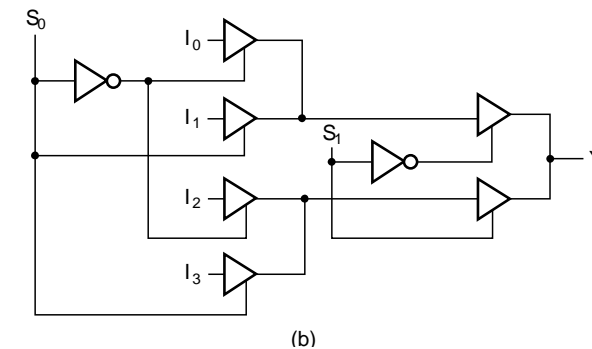

(b)

- Gate input cost = 14 compared to 22 (or 18) for gate implementation

36

Combinational Logic Implementation - Multiplexer Approach 1

- Implement m functions of n variables with:
 - Sum-of-minterms expressions
 - An m -wide 2^n -to-1-line multiplexer
- Design:
 - Find the truth table for the functions.
 - In the order they appear in the truth table:
 - Apply the function input variables to the multiplexer inputs S_{n-1}, \dots, S_0
 - Label the outputs of the multiplexer with the output variables
 - Value-fix the information inputs to the multiplexer using the values from the truth table (for don't cares, apply either 0 or 1)

37

Example: Gray to Binary Code

- Design a circuit to convert a 3-bit Gray code to a binary code
- The formulation gives the truth table on the right
- It is obvious from this table that $X = C$ and the Y and Z are more complex

Gray A B C	Binary x y z
0 0 0	0 0 0
1 0 0	0 0 1
1 1 0	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 1 1	1 0 1
1 0 1	1 1 0
0 0 1	1 1 1

38

Gray to Binary (continued)


- Rearrange the table so that the input combinations are in counting order
- Functions y and z can be implemented using a dual 8-to-1-line multiplexer by:

Gray A B C	Binary x y z
0 0 0	0 0 0
0 0 1	1 1 1
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	0 0 1
1 0 1	1 1 0
1 1 0	0 1 0
1 1 1	1 0 1

- connecting A , B , and C to the multiplexer select inputs
- placing y and z on the two multiplexer outputs
- connecting their respective truth table values to the inputs

39

Gray to Binary (continued)

 

- Note that the multiplexer with fixed inputs is identical to a ROM with 3-bit addresses and 2-bit data!

40

Combinational Logic Implementation - Multiplexer Approach 2

- Implement any m functions of $n + 1$ variables by using:
 - An m -wide 2^n -to-1-line multiplexer
 - A single inverter
- Design:
 - Find the truth table for the functions.
 - Based on the values of the first n variables, separate the truth table rows into pairs
 - For each pair and output, define a rudimentary function of the final variable (0, 1, X , \bar{X})
 - Using the first n variables as the index, value-fix the information inputs to the multiplexer with the corresponding rudimentary functions
 - Use the inverter to generate the rudimentary function \bar{X}

41

Example: Gray to Binary Code

- Design a circuit to convert a 3-bit Gray code to a binary code
- The formulation gives the truth table on the right
- It is obvious from this table that $X = C$ and the Y and Z are more complex

Gray A B C	Binary x y z
0 0 0	0 0 0
1 0 0	0 0 1
1 1 0	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 1 1	1 0 1
1 0 1	1 1 0
0 0 1	1 1 1

42

Gray to Binary (continued)


- Rearrange the table so that the input combinations are in counting order, pair rows, and find rudimentary functions

Gray A B C	Binary x y z	Rudimentary Functions of C for y	Rudimentary Functions of C for z
0 0 0	0 0 0	F = C	F = C
0 0 1	1 1 1		
0 1 0	0 1 1	F = \bar{C}	F = \bar{C}
0 1 1	1 0 0		
1 0 0	0 0 1	F = C	F = \bar{C}
1 0 1	1 1 0		
1 1 0	0 1 0	F = \bar{C}	F = C
1 1 1	1 0 1		

43

Gray to Binary (continued)

 - Assign the variables and functions to the multiplexer inputs:




- Note that this approach (Approach 2) reduces the cost by almost half compared to Approach 1.
- This result is no longer ROM-like
- Extending, a function of more than n variables is decomposed into several sub-functions defined on a subset of the variables. The multiplexer then selects among these sub-functions.

44

Additional Considerations

Non-Ideal Gate Behavior -- Delay


2.10

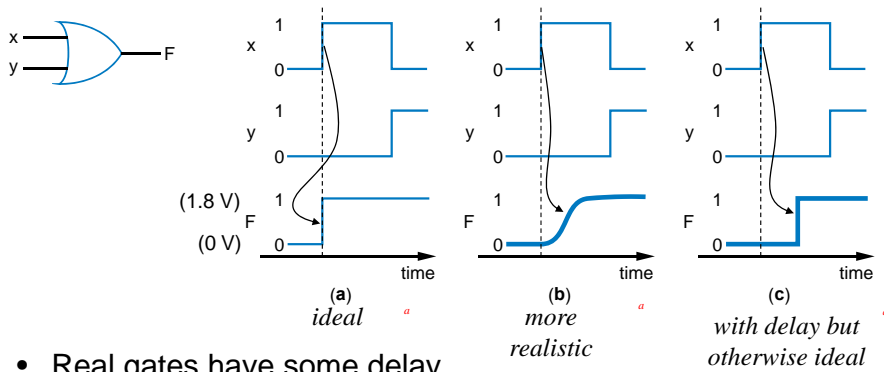

- Real gates have some delay
 - Outputs don't change immediately after inputs change

45

Circuit Delay and Critical Path

 


- Wires also have delay
- Assume gates and wires have delays as shown
- Path delay – time for input to affect output
- Critical path – path with longest path delay
- Circuit delay – delay of critical path

46


Active Low Inputs

 - Data inputs: flow through component (e.g., mux data input)
- Control input: influence component behavior
 - Normally active high – 1 causes input to carry out its purpose
 - Active low – Instead, 0 causes input to carry out its purpose
 - Example: 2x4 decoder with active low enable
 - 1 disables decoder, 0 enables
 - Drawn using inversion bubble



47

Schematic Capture and Simulation

 

- **Schematic capture**
 - Computer tool for user to capture logic circuit graphically
- **Simulator**
 - Computer tool to show what circuit outputs would be for given inputs
 - Outputs commonly displayed as **waveform**

48

Chapter Summary

- Combinational circuits
 - Circuit whose outputs are function of present inputs
 - No “state”
- Switches: Basic component in digital circuits
- Boolean logic gates: AND, OR, NOT – Better building block than switches
 - Enables use of Boolean algebra to design circuits
- Boolean algebra: Uses true/false variables/operators
- Representations of Boolean functions: Can translate among
- Combinational design process: Translate from equation (or table) to circuit through well-defined steps
- More gates: NAND, NOR, XOR, XNOR also useful
- Muxes and decoders: Additional useful combinational building blocks