

# COM 251 Logic Design and Circuits

## Register-Transfer Level (RTL) Design

Prof. Dr. Halûk Gümüşkaya

haluk.gumuskaya@gediz.edu.tr

haluk@gumuskaya.com http://www.gumuskaya.com

Computer Engineering Department

**GEDİZ**ÜNİVERSİTESİ  
izmir

Monday, December 12, 2011

1

## Acknowledgement

The slides have been based in-part upon original slides of a number of books including:


- *Digital Design with RTL Design, Verilog and VHDL*, 2nd ed., Frank Vahid, John Wiley, 2011.

2

## Introduction

 5.1

- Chpt 2
  - Capture Comb. behavior: Equations, truth tables
  - Convert to circuit: AND + OR + NOT → Comb. logic
- Chpt 3
  - Capture sequential behavior: FSMs
  - Convert to circuit: Register + Comb. logic → Controller
- Chpt 4
  - Datapath components, simple datapaths
- Chpt 5
  - Capture behavior: High-level state machine
  - Convert to circuit: Controller + Datapath → Processor
  - Known as “RTL” (register-transfer level) design



Levels of digital design abstraction

Processors:

- Programmable (microprocessor)
- Custom


Note: Slides with animation are denoted with a small red "a" near the animated items

3

## High-Level State Machines (HLSMs)

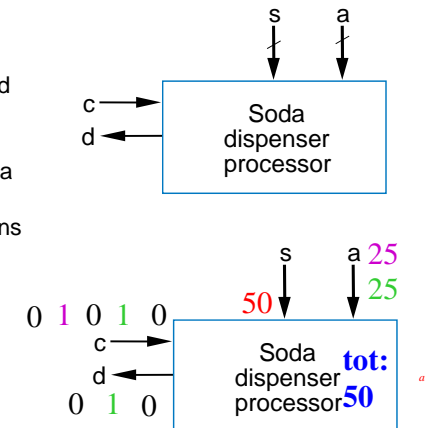5.2

- Some behaviors too complex for equations, truth tables, or FSMs
- Ex: Soda dispenser
  - c: bit input, 1 when coin deposited
  - a: 8-bit input having value of deposited coin
  - s: 8-bit input having cost of a soda
  - d: bit output, processor sets to 1 when total value of deposited coins equals or exceeds cost of a soda
- FSM can't represent...
  - 8-bit input/output
  - Storage of current total
  - Addition (e.g., 25 + 10)




4








# Example: Laser-Based Distance Measurer

 

- Once reflection detected (S), go to new state **S4**
  - Calculate distance
  - Assuming clock frequency is  $3 \times 10^8$ , *Dctr* holds number of meters, so  $Dreg := Dctr/2$
- After **S4**, go back to **S1** to wait for button again
   
# HLSM Actions: Updates Occur Next Clock Cycle

- Local storage updated on clock edges only
  - Enter state on clock edge
  - Storage writes in that state occur on *next* clock edge
  - Can think of as occurring on outgoing transitions
- **Thus**, transition conditions use the OLD value, not the newly-written value
  - Example:




(a)


(b)
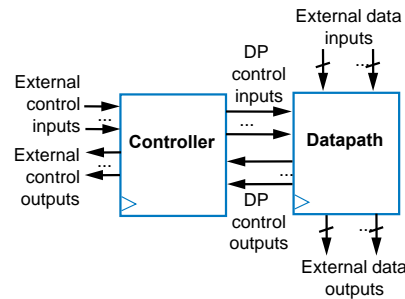
# RTL Design Process


- Capture behavior
- Convert to circuit
  - Need target architecture
  - Datapath capable of HLSM's data operations
  - Controller to control datapath



 
# Ctrl/DP Example for Earlier Cycles-High Counter




We created this HLSM earlier

 

(b)

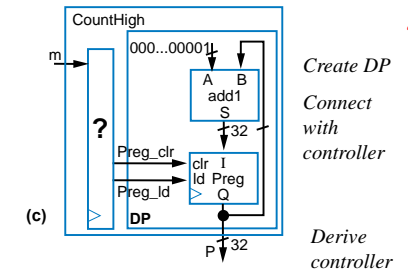

(c)

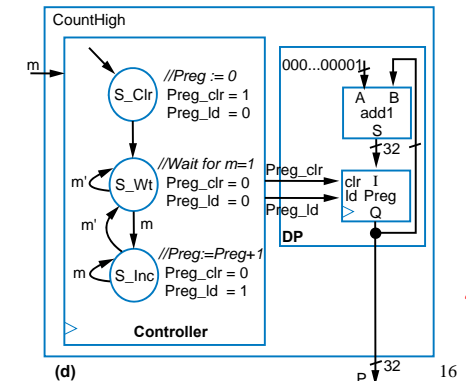


(d)

# RTL Design Process


Step	Description
<b>Step 1:</b> Capture behavior	<i>Capture a high-level state machine</i> Describe the system's desired behavior as a high-level state machine. The state machine consists of states and transitions. The state machine is "high-level" because the transition conditions and the state actions are more than just Boolean operations on single-bit inputs and outputs.
<b>2A</b>	<i>Create a datapath</i> Create a datapath to carry out the data operations of the high-level state machine.
<b>Step 2:</b> Convert to circuit	<i>Connect the datapath to a controller</i> Connect the datapath to a controller block. Connect external control inputs and outputs to the controller block.
<b>2B</b>	<i>Derive the controller's FSM</i> Convert the high-level state machine to a finite-state machine (FSM) for the controller, by replacing data operations with setting and reading of control signals to and from the datapath.
<b>2C</b>	<i>Derive the controller's FSM</i> Convert the high-level state machine to a finite-state machine (FSM) for the controller, by replacing data operations with setting and reading of control signals to and from the datapath.
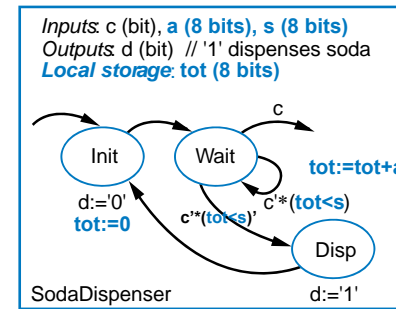
# Example: Soda Dispenser from Earlier


- Quick overview example. More details of each step to come.



Step 1

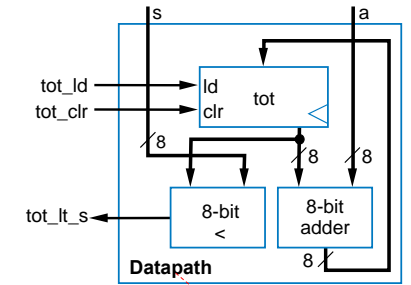


Step 2A

 


Step 2B
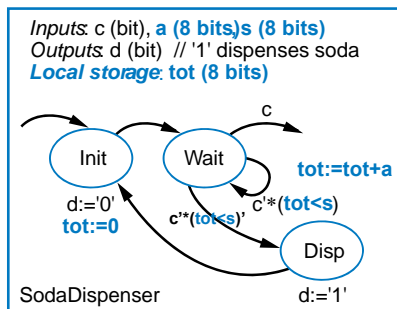
# Example: Soda Dispenser


- Quick overview example. More details of each step to come.



Step 1

 

Step 2B

 

Step 2C

# Example: Soda Dispenser

- Quick overview example. More details of each step to come.


	s1	s0	c	tot_lt_s	n1	n0	d	tot_ld	tot_clr
Init	0	0	0	0	0	1	0	0	1
	0	0	0	1	0	1	0	0	1
	0	0	1	0	0	1	0	0	1
	0	0	1	1	0	1	0	0	1
Wait	0	1	0	0	1	1	0	0	0
	0	1	0	1	0	1	0	0	0
	0	1	1	0	1	0	0	0	0
	0	1	1	1	1	0	0	0	0
Add	1	0	0	0	0	1	0	1	0
	...	...	...	...	...	...	...	...	...
Disp	1	1	0	0	0	0	1	0	0
	...	...	...	...	...	...	...	...	...

Step 2C

Use controller design process (Ch3) to complete the design

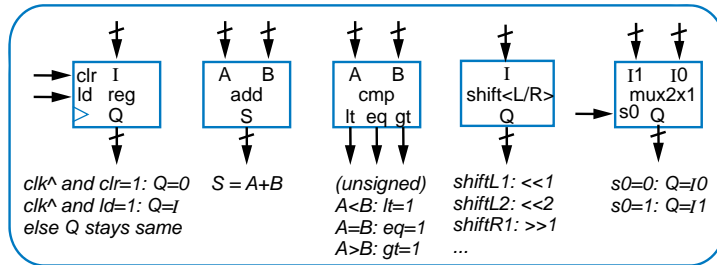
## RTL Design Process—Step 2A: Create a datapath

- Sub-steps
  - HLSM data inputs/outputs → Datapath inputs/outputs.
  - HLSM local storage item → Instantiated register
    - "Instantiate": Add new component ("instance") to design
  - Each HLSM state action and transition condition data computation → Datapath components and connections
    - Also instantiate multiplexers as needed
- Need component library from which to choose




21
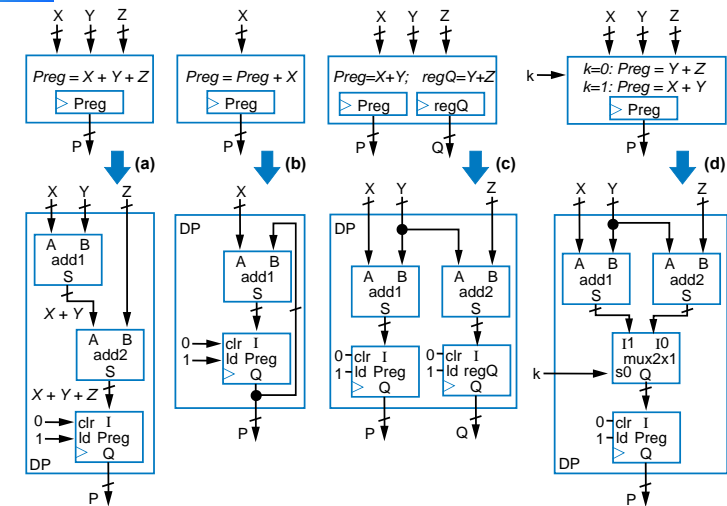
## Step 2A: Create a Datapath—Simple Examples




22
 
## Laser-Based Distance Measurer—Step 2A: Create a Datapath




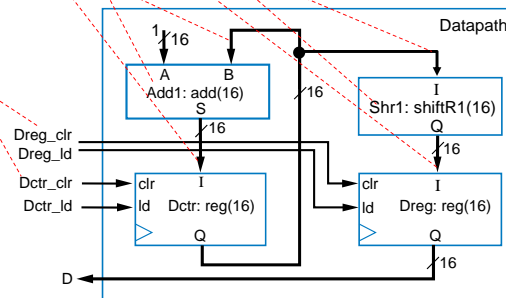- HLSM data I/O → DP I/O
- HLSM local storage → reg
- HLSM state action and transition condition data computation → Datapath components and connections




23
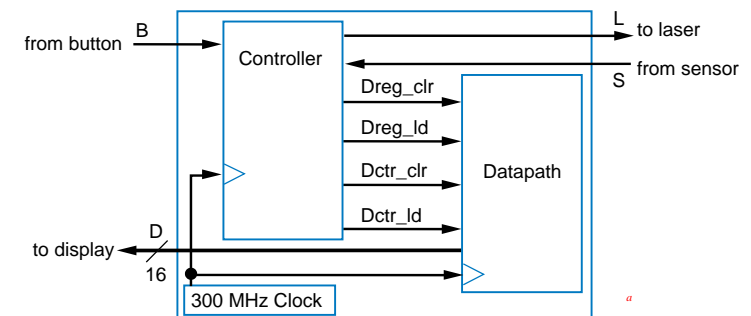
## Laser-Based Distance Measurer—Step 2B: Connecting the Datapath to a Controller



24

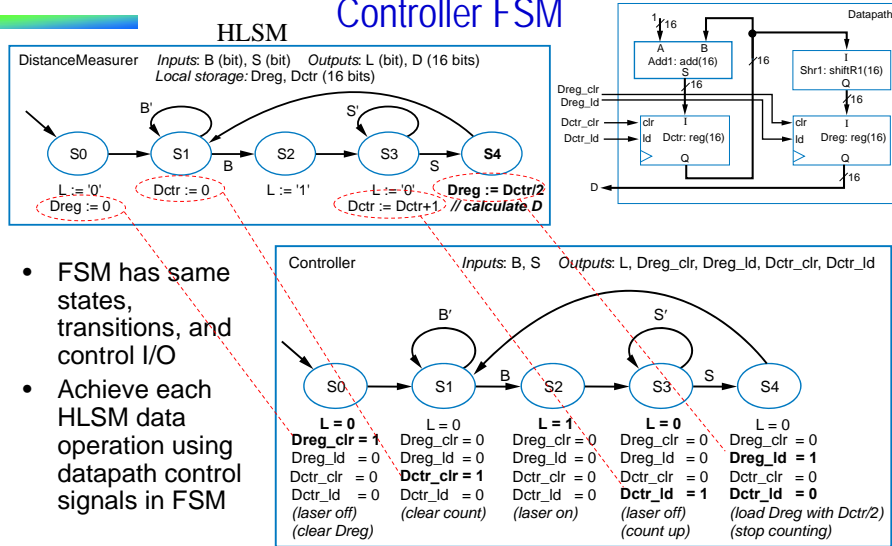
## Laser-Based Distance Measurer—Step 2C: Derive the Controller FSM



- FSM has same states, transitions, and control I/O
- Achieve each HLSM data operation using datapath control signals in FSM

25
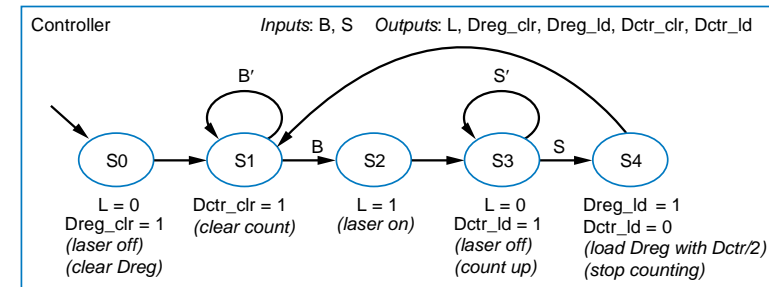
## Laser-Based Distance Measurer—Step 2C: Derive the Controller FSM



- Same FSM, using convention of unassigned outputs implicitly assigned 0


*Some assignments to 0 still shown, due to their importance in understanding desired controller behavior*

26

5.4

## More RTL Design

- Additional datapath components

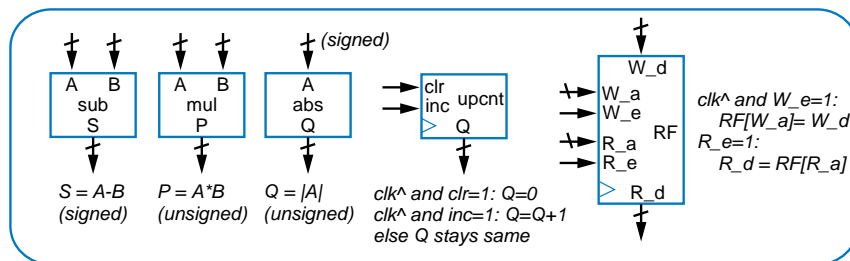


27

## RTL Design Involving Register File or Memory


- HLSM *array*: Ordered list of items
  - Ex: Local storage:  $A[4]$  (8-bit) – 4 8-bit items
  - Accessed using notation " $A[i]$ ",  $i$  is *index*
  - $A[0] := 9$ ;  $A[1] := 8$ ;  $A[2] := 7$ ;  $A[3] := 22$ 
    - Array contents now:  $\langle 9, 8, 7, 22 \rangle$
    - $X := A[1]$  will set  $X$  to 8
    - Note: First element's index is 0
- Array can be mapped to instantiated register file or memory

28


## Simple Array Example

 

(a)

 


(c)

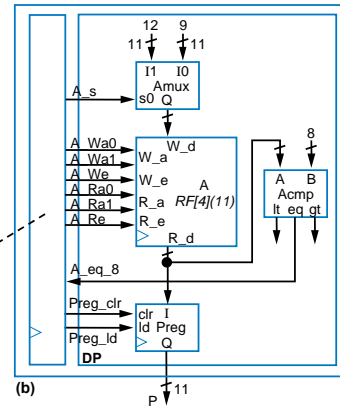


(b)
 
## RTL Example: Video Compression – Sum of Absolute Differences




- Video is a series of frames (e.g., 30 per second)
- Most frames similar to previous frame
  - Compression idea: just send difference from previous frame
 
## RTL Example: Video Compression – Sum of Absolute Differences




- Need to quickly determine whether two frames are similar enough to just send difference for second frame
  - Compare corresponding 16x16 “blocks”
    - Treat 16x16 block as 256-byte array
  - Compute the absolute value of the difference of each array item
  - Sum those differences – if above a threshold, send complete frame for second frame; if below, can use difference method (using another technique, not described)
 
## Array Example: Video Compression—Sum-of-Absolute Differences



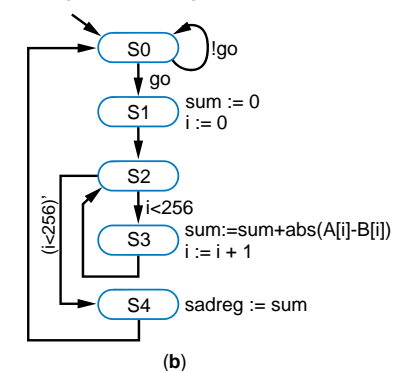
Inputs: A, B [256](8 bits); go (bit)  
Outputs: sad (32 bits)  
Local storage: sum, sadreg (32 bits); i (9 bits)



- **S0**: wait for go
- **S1**: initialize *sum* and *index*
- **S2**: check if done ( (*i*<256) )
- **S3**: add difference to *sum*, increment index
- **S4**: done, write to output *sad\_reg*

Inputs: A, B [256](8 bits); go (bit)  
 Outputs: sad (32 bits)  
 Local storage: sum, sadreg (32 bits); i (9 bits)

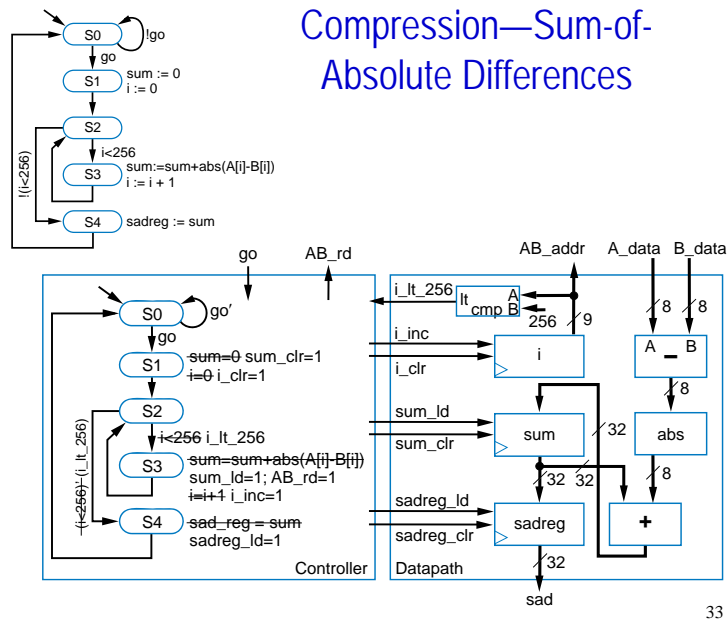
## Array Example: Video Compression—Sum-of-Absolute Differences



33
 
## Circuit vs. Microprocessor


- Circuit: Two states (**S2** & **S3**) for each  $i$ , 256  $i$ 's  $\rightarrow$  512 clock cycles
- Microprocessor: Loop (for  $i = 1$  to 256), but for each  $i$ , must move memory to local registers, subtract, compute absolute value, add to sum, increment  $i$  – say 6 cycles per array item  $\rightarrow 256 \cdot 6 = 1536$  cycles
- Circuit is about 3 times (300%) faster (assuming equal cycle lengths)
- Later, we'll see how to build SAD circuit that is *much* faster



34

## Common RTL Design Pitfall Involving Storage Updates

 
- Questions
  - Value of Q after state A?
  - Final state is C or D?
- Answers
  - Q is NOT 99 after state A
  - Q is 99 in state B, so final state is C
  - Storage update actions in state occur *simultaneously* on *next* clock edge
    - Thus, order actions are written is irrelevant
    - A's actions same if:
      - $Q := R$   $R := 99$  or
      - $R := 99$   $Q := R$



35
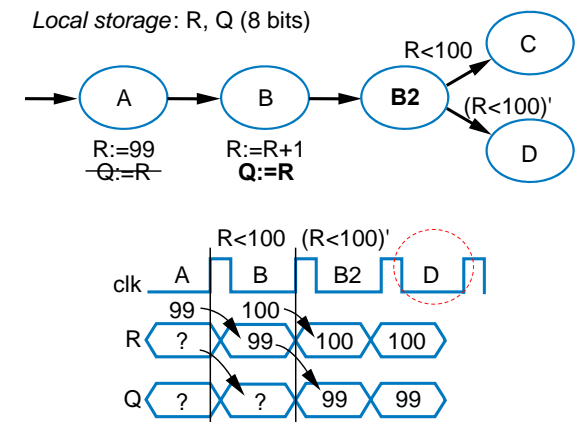
## Common RTL Design Pitfall Involving Storage Updates



- New HLSM using extra state so read of R occurs after write of R




36
  
## RTL Design Involving a Timer

- Commonly need explicit time intervals
  - Ex: Repeatedly blink LED on 1 second, off 1 second
- Pre-instantiate timer that HLSM can then use



(a) Pre-instantiated timer


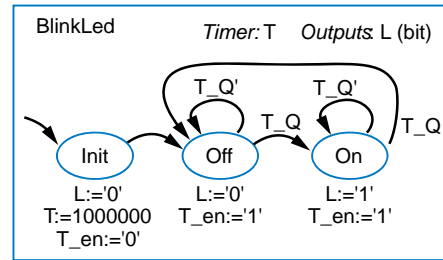


(b) HLSM making use of timer

37
 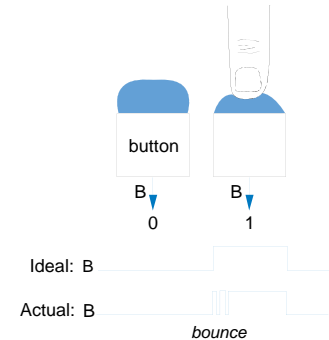
## Button Debouncing


- Press button
  - Ideally, output changes to 1
  - Actually, output bounces
    - Due to mechanical reasons
    - Like ball bouncing when dropped to floor
- Digital circuit can convert actual signal closer to ideal signal



38
 
## Data Dominated RTL Design Example

- Data dominated design: Extensive DP, simple controller
- Control dominated design: Complex controller, simple DP
- Example: Filter
  - Converts digital input stream to new digital output stream
  - Ex: Remove noise
    - 180, 180, 181, 180, 240, 180, 181
    - 240 is probably noise, filter might replace by 181
  - Simple filter: Output average of last  $N$  values
    - Small  $N$ : less filtering
    - Large  $N$ : more filtering, but less sharp output




39
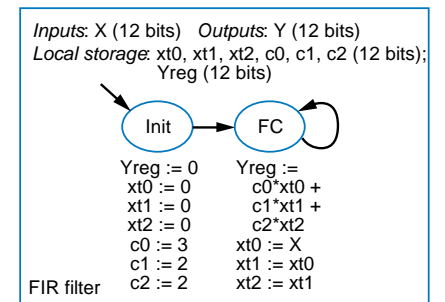
## Data Dominated RTL Design Example: FIR Filter

- FIR filter
  - “Finite Impulse Response”
  - Simply a configurable weighted sum of past input values
  - $y(t) = c_0*x(t) + c_1*x(t-1) + c_2*x(t-2)$ 
    - Above known as “3 tap”
    - Tens of taps more common
    - Very general filter – User sets the constants ( $c_0, c_1, c_2$ ) to define specific filter
- RTL design
  - Step 1: Create HLSM
    - Very simple states/transitions




$$y(t) = c_0*x(t) + c_1*x(t-1) + c_2*x(t-2)$$




Assume constants set to 3, 2, and 2

40

## FIR Filter

 

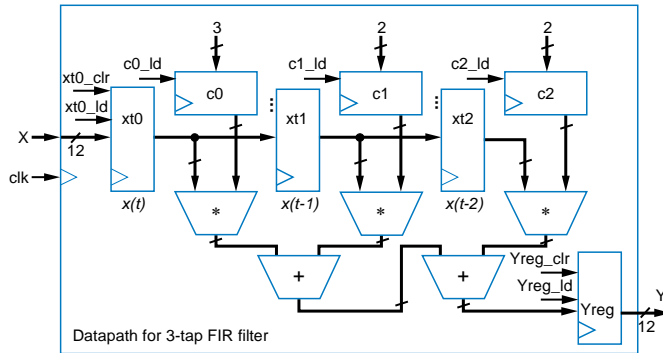- Step 2A: Create datapath
- Step 2B: Connect Ctrlr/DP (as earlier examples)
- Step 2C: Derive FSM
  - Set clr and ld lines appropriately



41

## Circuit vs. Microprocessor


$$y(t) = c0*x(t) + c1*x(t-1) + c2*x(t-2)$$

- Comparing the FIR circuit to microprocessor instructions
  - Microprocessor
    - 100-tap filter: 100 multiplications, 100 additions. Say 2 instructions per multiplication, 2 per addition. Say 10 ns per instruction.
    - $(100*2 + 100*2)*10 = 4000$  ns
  - Circuit
    - Assume adder has 2 ns delay, multiplier has 20 ns delay
    - Longest path goes through one multiplier and two adders
      - $20 + 2 + 2 = 24$  ns delay
    - 100-tap filter, following design on previous slide, would have about a 34 ns delay: 1 multiplier and 7 adders on longest path
  - Circuit is more than 100 times faster (4000/34). Wow.

42
 
## Determining Clock Frequency


- Designers of digital circuits often want fastest performance
  - Means want high clock frequency
- Frequency limited by **longest register-to-register delay**
  - Known as **critical path**
  - If clock is any faster, incorrect data may be stored into register
  - Longest path on right is 2 ns
    - Ignoring wire delays, and register setup and hold times, for simplicity



43

## Critical Path

 
- Example shows four paths
  - a to c through +: 2 ns
  - a to d through + and \*: 7 ns
  - b to d through + and \*: 7 ns
  - b to d through \*: 5 ns
- Longest path is thus 7 ns
- Fastest frequency
  - $1 / 7 \text{ ns} = 142 \text{ MHz}$



44
 
## Critical Path Considering Wire Delays


- Real wires have delay too
  - Must include in critical path
- Example shows two paths
  - Each is  $0.5 + 2 + 0.5 = 3$  ns
- Trend
  - 1980s/1990s: Wire delays were tiny compared to logic delays
  - But wire delays not shrinking as fast as logic delays
    - Wire delays may even be greater than logic delays!
- Must also consider register setup and hold times, also add to path
- Then add some time to the computed path, just to be safe
  - e.g., if path is 3 ns, say 4 ns instead



45
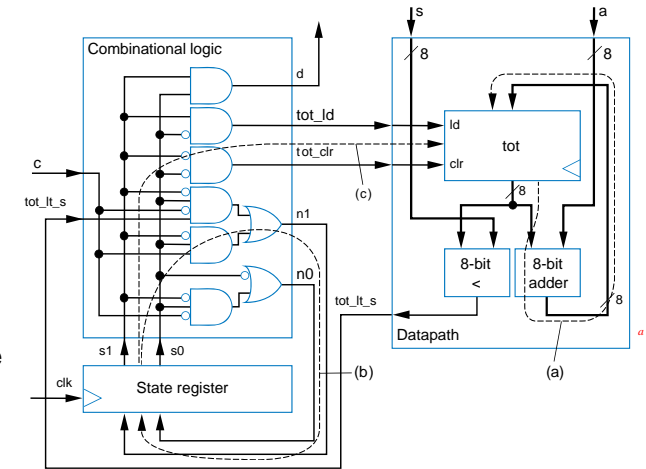
## A Circuit May Have Numerous Paths

- Paths can exist
  - In the datapath
  - In the controller
  - Between the controller and datapath
  - May be hundreds or thousands of paths
- Timing analysis tools that evaluate all possible paths automatically very helpful



46


## Behavioral Level Design: C to Gates

5.6

Inputs: A, B [256](8 bits); go (bit)  
 Outputs: sad (32 bits)  
 Local storage: sum, sadreg (32 bits); i (9 bits)

C code
 
```
int SAD (byte A[256], byte B[256]) // not quite C syntax
{
    uint sum; short uint i;
    sum = 0;
    i = 0;
    while (i < 256) {
        sum = sum + abs(A[i] - B[i]);
        i = i + 1;
    }
    return sum;
}
```




- Earlier sum-of-absolute-differences example
  - Started with high-level state machine
  - C code is an even better starting point -- easier to understand

47
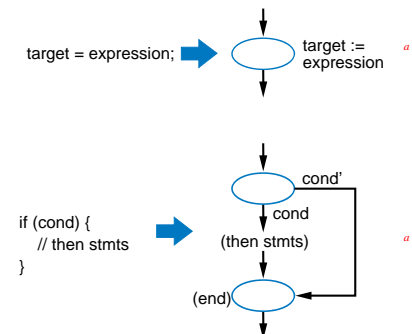
## Converting from C to High-Level State Machine

- Convert each C construct to equivalent states and transitions
- Assignment statement
  - Becomes one state with assignment
- If-then statement
  - Becomes state with condition check, transitioning to "then" statements if condition true, otherwise to ending state
    - "then" statements would also be converted to states




48
 
## Converting from C to High-Level State Machine


- If-then-else**

- Becomes state with condition check, transitioning to “then” statements if condition true, or to “else” statements if condition false



- While loop statement**

 - Becomes state with condition check, transitioning to while loop’s statements if true, then transitioning back to condition check




## Simple Example of Converting from C to High-Level State Machine

Inputs: uint X, Y  
Outputs: uint Max

```

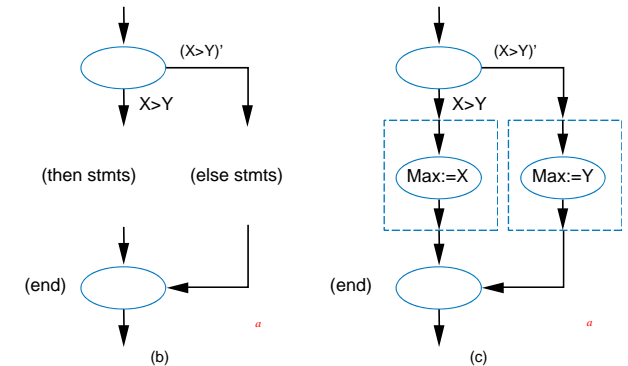if (X > Y) {
  Max = X;
}
else {
  Max = Y;
}
    
```




- Simple example: Computing the maximum of two numbers
  - Convert if-then-else statement to states (b)
  - Then convert assignment statements to states (c)

## Example: SAD C code to HLMS

```


Inputs: byte A[256], B[256]
bit go;
Output: int sad
main()
{
  uint sum; short uint i;
  while (1) {
    while (!go);
    sum = 0;
    i = 0;
    while (i < 256) {
      sum = sum + abs(A[i] - B[i]);
      i = i + 1;
    }
    sad = sum;
  }
}
    
```

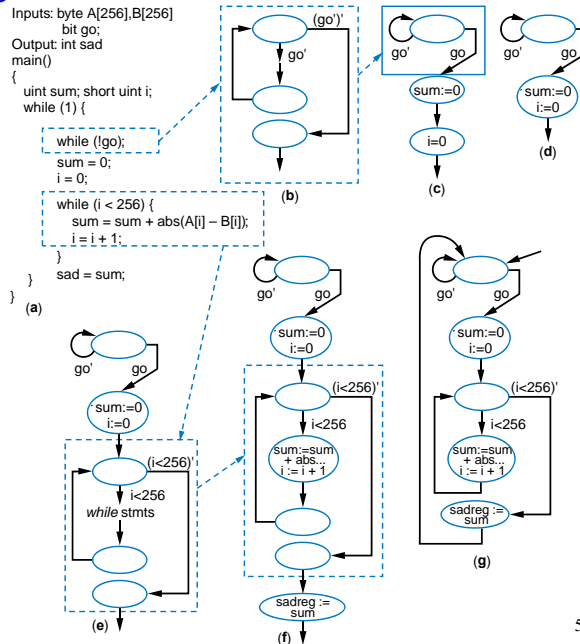- Convert each construct to states
  - Simplify, e.g., merge states
- RTL design process to convert to circuit
- Can thus convert C to circuit using straightforward process
  - Actually, subset of C (not all C constructs easily convertible)
  - Can use language other than C



 
## Memory Components

- RTL design instantiates datapath components to create datapath, controlled by a controller
  - Some components are used outside the controller and DP
- **MxN memory**
  - M words, N bits wide each
- Several varieties of memory, which we now introduce



 
# Random Access Memory (RAM)

- RAM – Readable and writable memory
  - “Random access memory”
    - Strange name—Created several decades ago to contrast with sequentially-accessed storage like tape drives
  - Logically same as register file—Memory with address inputs, data inputs/outputs, and control
    - RAM usually one port; RF usually two or more
  - RAM vs. RF
    - RAM typically larger than *about* 512 or 1024 words
    - RAM typically stores bits using a bit storage approach that is more efficient than a flip-flop
    - RAM typically implemented on a chip in a square rather than rectangular shape—keeps longest wires (hence delay) short




Register file from Chpt. 4

 


RAM block symbol

# RAM Internal Structure



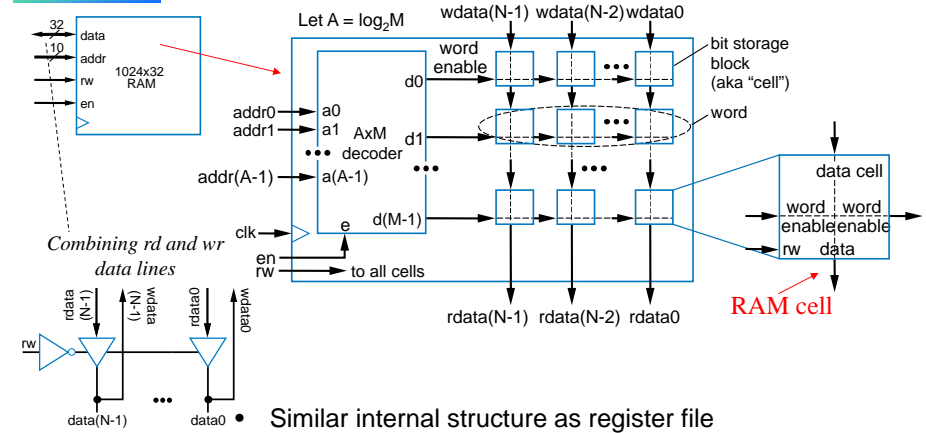


- Similar internal structure as register file
  - Decoder enables appropriate word based on address inputs
  - rw controls whether cell is written or read
  - rd and wr data lines typically combined
  - Let's see what's inside each RAM cell


# Static RAM (SRAM)

 


- “Static” RAM cell
  - 6 transistors (recall inverter is 2 transistors)
  - Writing this cell
    - word enable input comes from decoder
    - When 0, value *d* loops around inverters
      - That loop is where a bit stays stored
    - When 1, the *data* bit value enters the loop
      - *data* is the bit to be stored in this cell
      - *data'* enters on other side
      - Example shows a “1” being written into cell

   


# Static RAM (SRAM)

 

- “Static” RAM cell
  - Reading this cell
    - Somewhat trickier
    - When rw set to read, the RAM logic sets both *data* and *data'* to 1
    - The stored bit *d* will pull either the left line or the right bit down slightly below 1
    - “Sense amplifiers” detect which side is slightly pulled down
  - The electrical description of SRAM is really beyond our scope – just general idea here, mainly to contrast with *DRAM*...

 

## Dynamic RAM (DRAM)

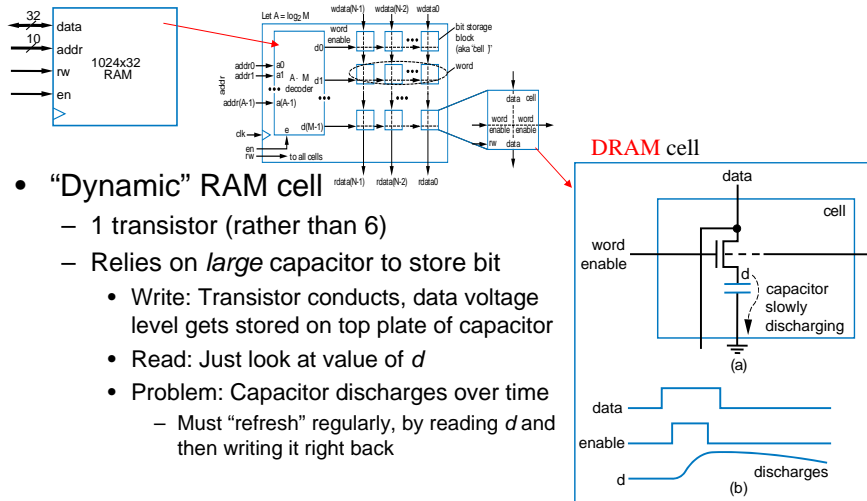


- “Dynamic” RAM cell
  - 1 transistor (rather than 6)
  - Relies on *large* capacitor to store bit
    - Write: Transistor conducts, data voltage level gets stored on top plate of capacitor
    - Read: Just look at value of *d*
    - Problem: Capacitor discharges over time
      - Must “refresh” regularly, by reading *d* and then writing it right back

57
 
## Comparing Memory Types


- Register file
  - Fastest
  - But biggest size
- SRAM
  - Fast
  - More compact than register file
- DRAM
  - Slowest
    - And refreshing takes time
  - But very compact
- Use register file for small items, SRAM for large items, and DRAM for huge items
  - Note: DRAM's big capacitor requires a special chip design process, so DRAM is often a separate chip



Size comparison for same number of bits (not to scale)

58


## Reading and Writing a RAM

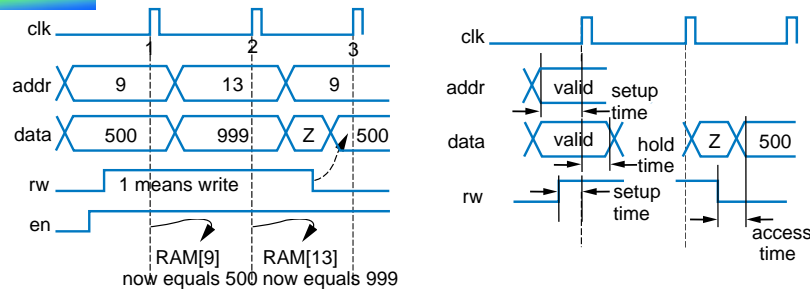

- Writing
  - Put address on *addr* lines, data on *data* lines, set *rw=1*, *en=1*
- Reading
  - Set *addr* and *en* lines, but put nothing (Z) on *data* lines, set *rw=0*
  - Data will appear on *data* lines
- Don't forget to obey setup and hold times
  - In short – keep inputs stable before and after a clock edge

59

## RAM Example: Digital Sound Recorder

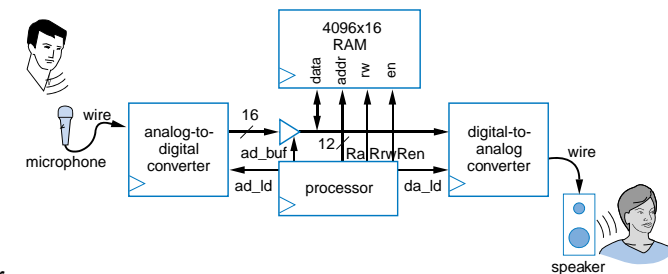


- Behavior
  - Record: Digitize sound, store as series of 4096 12-bit digital values in RAM
    - We'll use a 4096x16 RAM (12-bit wide RAM not common)
  - Play back later
  - Common behavior in telephone answering machine, toys, voice recorders
- To record, processor should read a-to-d, store read values into successive RAM words
  - To play, processor should read successive RAM words and enable d-to-a

60
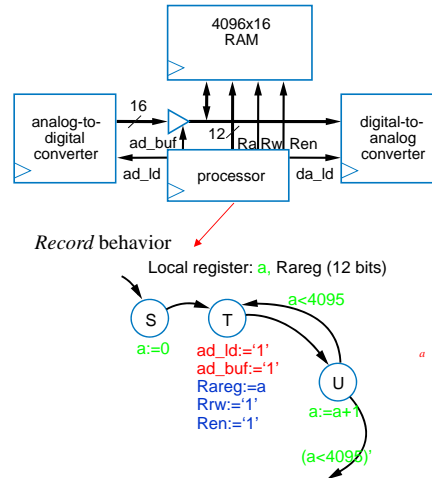
## RAM Example: Digital Sound Recorder


- RTL design of processor
  - Create HLSM
  - Begin with the *record* behavior
  - Create local storage *a*
    - Stores current address, ranges from 0 to 4095 (thus need 12 bits)
  - Create state machine that counts from 0 to 4095 using *a*
    - For each *a*
      - Read analog-to-digital conv.
        - »  $ad\_ld:=1, ad\_buf:=1$
      - Write to RAM at address *a*
        - »  $Rareg:=a, Rrw:=1, Ren:=1$



61
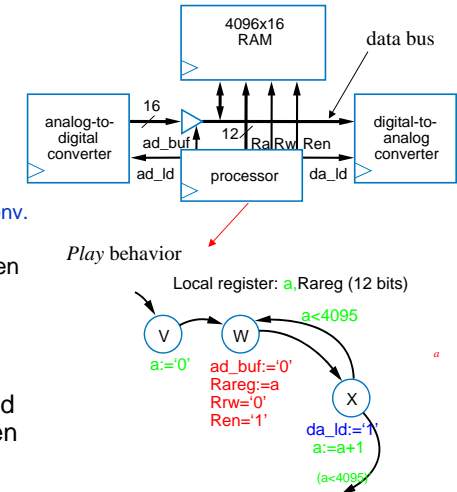
## RAM Example: Digital Sound Recorder



- Now create *play* behavior
- Use local register *a* again, create state machine that counts from 0 to 4095 again
  - For each *a*
    - Read RAM
      - »  $Rareg:=a, Rrw:=0, Ren:=1$
    - Write to digital-to-analog conv.
      - »  $ad\_buf:=1, da\_ld:=1$
  - Note: Must write d-to-a one cycle *after* reading RAM, when the read data is available on the data bus
- The record and play state machines would be parts of a larger state machine controlled by signals that determine when to record or play



62

  
## Read-Only Memory – ROM

- Memory that can only be read from, not written to
  - Data lines are output only
  - No need for *rw* input
- Advantages over RAM
  - Compact: May be smaller
  - **Nonvolatile**: Saves bits even if power supply is turned off
  - Speed: May be faster (especially than DRAM)
  - Low power: Doesn't need power supply to save bits, so can extend battery life
- Choose ROM over RAM if stored data won't change (or won't change often)
  - For example, a table of Celsius to Fahrenheit conversions in a digital thermometer



63

## Read-Only Memory – ROM

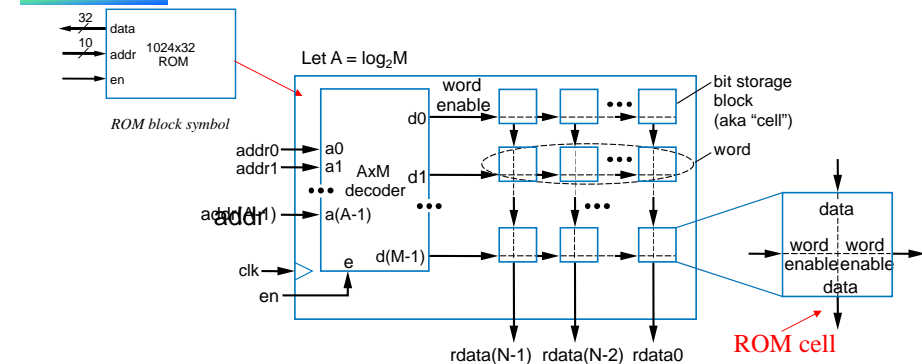


- Internal logical structure similar to RAM, without the data input lines

64
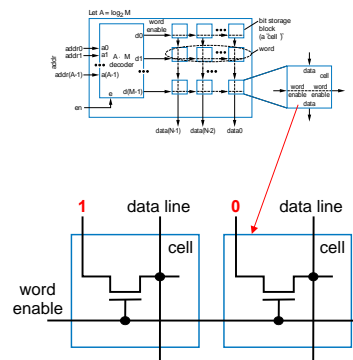
## ROM Types

- If a ROM can only be read, how are the stored bits stored in the first place?
  - Storing bits in a ROM known as *programming*
  - Several methods
- **Mask-programmed ROM**
  - Bits are hardwired as 0s or 1s during chip manufacturing
    - 2-bit word on right stores “10”
    - word enable (from decoder) simply passes the hardwired value through transistor
  - Notice how compact, and fast, this memory would be




65

## ROM Types
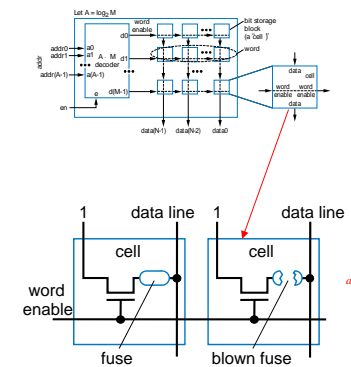
### • Fuse-Based Programmable ROM

- Each cell has a fuse
- A special device, known as a programmer, blows certain fuses (using higher-than-normal voltage)
  - Those cells will be read as 0s (involving some special electronics)
  - Cells with unblown fuses will be read as 1s
  - 2-bit word on right stores “10”
- Also known as **One-Time Programmable (OTP) ROM**




66

## ROM Types
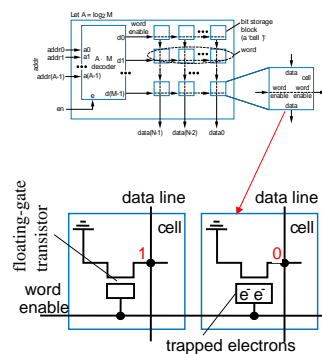
### • Erasable Programmable ROM (EPROM)

- Uses “floating-gate transistor” in each cell
- Special programmer device uses higher-than-normal voltage to cause electrons to *tunnel* into the gate
  - Electrons become trapped in the gate
  - Only done for cells that should store 0
  - Other cells (without electrons trapped in gate) will be 1
    - 2-bit word on right stores “10”
  - Details beyond our scope – just general idea is necessary here
- To erase, shine ultraviolet light onto chip
  - Gives trapped electrons energy to escape
  - Requires chip package to have window




67

## ROM Types

 
### • Electronically-Erasable Programmable ROM (EEPROM)

- Similar to EPROM
  - Uses floating-gate transistor, electronic programming to trap electrons in certain cells
- But erasing done *electronically*, not using UV light
- Erasing done one word at a time
- **Flash memory**
  - Like EEPROM, but all words (or large blocks of words) can be erased *simultaneously*
  - Became very common starting in late 1990s
- Both types are *in-system programmable*
  - Can be programmed with new stored bits while in the system in which the ROM operates
  - Requires bi-directional data lines, and write control input
  - Also need busy output to indicate that erasing is in progress – erasing takes some time



68


## ROM Example: Talking Doll

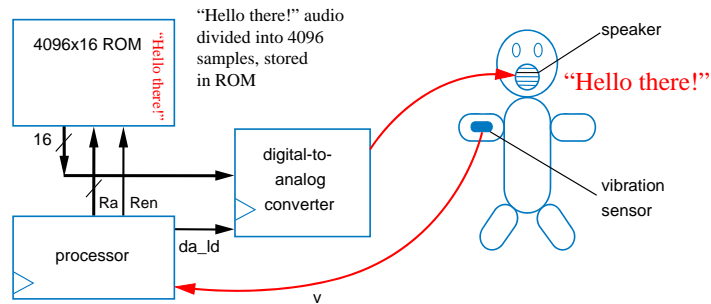

- Doll plays prerecorded message, triggered by vibration
  - Message must be stored without power supply → Use a ROM, not a RAM, because ROM is nonvolatile
    - And because message will never change, may use a mask-programmed ROM or OTP ROM
  - Processor should wait for vibration ( $v=1$ ), then read words 0 to 4095 from the ROM, writing each to the d-to-a

69

## ROM Example: Talking Doll

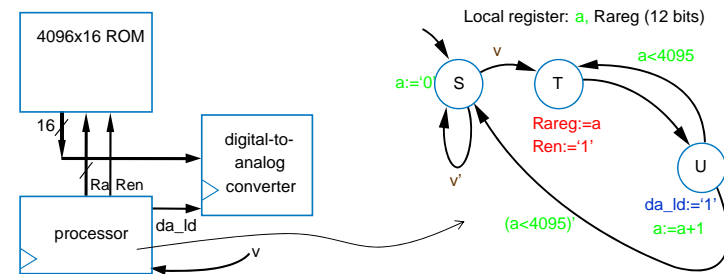


- HLSM
  - Create state machine that waits for  $v=1$ , and then counts from 0 to 4095 using a local storage  $a$
  - For each  $a$ , read ROM, write to digital-to-analog converter

70

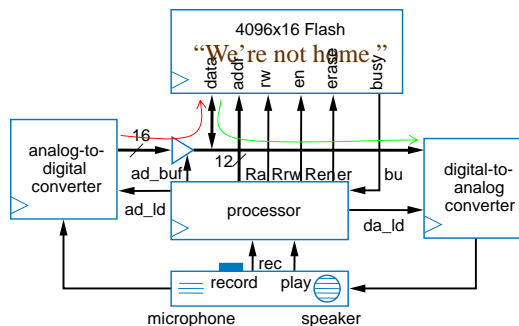
## ROM Example: Digital Telephone Answering Machine Using a Flash Memory

- Want to record the outgoing announcement
  - When  $rec=1$ , record digitized sound in locations 0 to 4095
  - When  $play=1$ , play those stored sounds to digital-to-analog converter
- What type of memory?
  - Should store without power supply – ROM, not RAM
  - Should be in-system programmable – EEPROM or Flash, not EPROM, OTP ROM, or mask-programmed ROM
  - Will always erase entire memory when reprogramming – Flash better than EEPROM


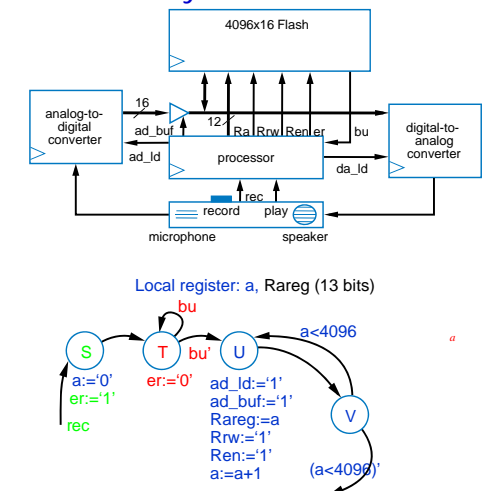
## ROM Example: Digital Telephone Answering Machine Using a Flash Memory

- HLSM
  - Once  $rec=1$ , begin erasing flash by setting  $er=1$
  - Wait for flash to finish erasing by waiting for  $bu=0$
  - Execute loop that sets local register  $a$  from 0 to 4095, reading analog-to-digital converter and writing to flash for each  $a$




71

72

 
## Blurring of Distinction Between ROM and RAM

- We said that
  - RAM is readable and writable
  - ROM is read-only
- But some ROMs act almost like RAMs
  - EEPROM and Flash are in-system programmable
    - Essentially means that writes are slow
      - Also, number of writes may be limited (perhaps a few million times)
- And, some RAMs act almost like ROMs
  - Non-volatile RAMs: Can save their data without the power supply
    - One type: Built-in battery, may work for up to 10 years
    - Another type: Includes ROM backup for RAM – controller writes RAM contents to ROM before turning off
- New memory technologies evolving that merge RAM and ROM benefits
  - e.g., MRAM
- Bottom line
  - Lot of choices available to designer, must find best fit with design goals



 
## Queues (FIFOs)

- A queue is another component sometimes used during RTL design
- Queue:** A list written to at the back, from read from the front
  - Like a list of waiting restaurant customers
- Writing called a **push**, reading called a **pop**
- Because first item written into a queue will be the first item read out, also called a **FIFO** (first-in-first-out)



 
## Queues

- Queue has addresses, and two pointers: **rear** and **front**
  - Initially both point to 0
- Push (write)
  - Item written to address pointed to by **rear**
  - rear** incremented
- Pop (read)
  - Item read from address pointed to by **front**
  - front** incremented
- If front or rear reaches 7, next (incremented) value should be 0 (for a queue with addresses 0 to 7)



 
## Queues

- Treat memory as a circle
  - If front or rear reaches 7, next (incremented) value should be 0 rather than 8 (for a queue with addresses 0 to 7)
- Two conditions of interest
  - Full queue – no room for more items
    - In 8-entry queue, means 8 items present
    - No further pushes allowed until a pop occurs
    - Causes front=rear
  - Empty queue – no items
    - No pops allowed until a push occurs
    - Causes front=rear
  - Both conditions have front=rear
    - To detect whether front=rear means full or empty, need state machine that detects if previous operation was push or pop, sets full or empty output signal (respectively)


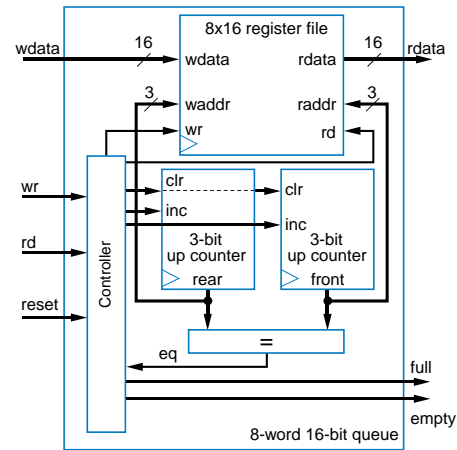
## Queue Implementation

- Can use register file for item storage
- Implement *rear* and *front* using up counters
  - rear used as register file's write address, front as read address
- Simple controller would set control lines for pushes and pops, and also detect full and empty situations
  - FSM for controller not shown



77


## Common Uses of a Queue

- Computer keyboard
  - Pushes pressed keys onto queue, meanwhile pops and sends to computer
- Digital video recorder
  - Pushes captured frames, meanwhile pops frames, compresses them, and stores them
- Computer network routers
  - Pushes incoming packets onto queue, meanwhile pops packets, processes destination information, and forwards each packet out over appropriate port

78

## Queue Usage Example


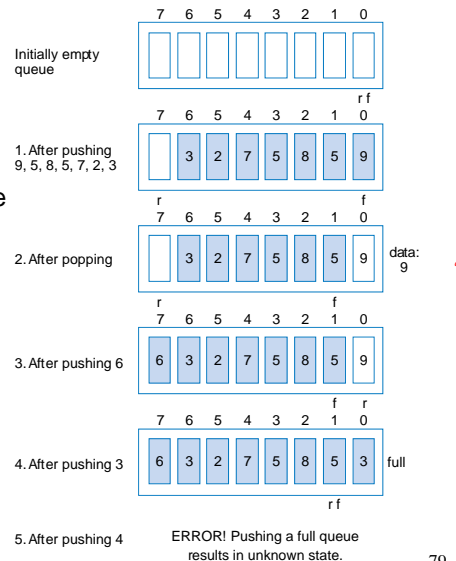
- Example series of pushes and pops
  - Note how rear and front pointers move
  - Note that popping doesn't really remove the data from the queue, but that data is no longer accessible
  - Note how rear (and front) wraps around from address 7 to 0
- Note: pushing a full queue is an error
  - So is popping an empty queue



79
  
## Multiple Processors

- Using multiple processors can ease design
  - Keeps distinct behaviors separate
  - Ex: Laser-based distance measurer with button debounce
    - Use two processors
  - Ex: Code detector with button press synchronizers (BPS)
    - BPS processor for each input, plus CodeDetector processor



5.9

80

## Interfacing Multiple Processors


- Use signal, register, or other component outside processors
  - Known as *global*
- Common methods use global...
  - control signal, data signal, register, register file, queue
- Typically all multiple processors and clocked globals use same clock
  - *Synchronized*

81
 
## Ex: Temperature Statistics with Multiple Processors

- 16-bit unsigned input T from temperature sensor, 16-bit output A. Sample T every 1 second. Compute output A every minute, should equal average of most recent 64 samples.
- Single HLSM: Complicated
- Instead, two HLSMs (and hence two processors) and shared register file
  - Tsample HLSM: Store T into successive RF address, once per sec.
  - Avg HLSM: Compute and output average of all 64 RF words, once per min.
  - Note that each uses distinct timer


Keeping the sampling and averaging behaviors separate leads to simple design



82
 
## Ex: Digital Camera with Mult. Processors and Queue



- Read and Compress processors (Ch 1)
  - Compress may take longer, depends on picture
  - Use queue, read can push additional pics (up to 8)
  - Likewise, use queue between Compress and Store



83
  
## Hierarchy – A Key Design Concept

- Hierarchy
  - Organization with few items at the top, with each item decomposed into other items
  - Common example: Country
    - 1 item at top (the country)
    - Country item decomposed into state/province items
    - Each state/province item decomposed into city items
- Hierarchy helps us **manage complexity**
  - To go from transistors to gates, muxes, decoders, registers, ALUs, controllers, datapaths, memories, queues, etc.
  - Imagine trying to comprehend a controller and datapath at the level of gates



Map showing just top two levels of hierarchy


5.10

84
 
## Hierarchy and Abstraction

- Abstraction



- Hierarchy often involves not just grouping items into a new item, but also associating higher-level behavior with the new item, known as *abstraction*
  - Ex: 8-bit adder has understandable high-level behavior—adds two 8-bit binary numbers
- Frees designer from having to remember, or even understand, the lower-level details



85
  
## Hierarchy and Composing Larger Components from Smaller Versions


- A common task is to compose smaller components into a larger one
  - Gates: Suppose you have plenty of 3-input AND gates, but need a 9-input AND gate
    - Can simply compose the 9-input gate from several 3-input gates
  - Muxes: Suppose you have 4x1 and 2x1 muxes, but need an 8x1 mux
    - s2 selects either top or bottom 4x1
    - s1s0 select particular 4x1 input
    - Implements 8x1 mux – 8 data inputs, 3 selects, one output



86
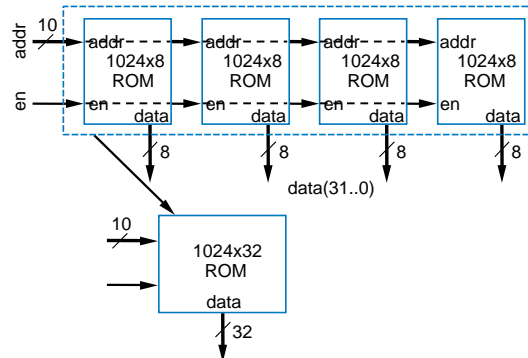
## Hierarchy and Composing Larger Components from Smaller Versions



- Composing memory very common
- Making memory words wider
  - Easy – just place memories side-by-side until desired width obtained
  - Share address/control lines, concatenate data lines
  - Example: Compose 1024x8 ROMs into 1024x32 ROM



87
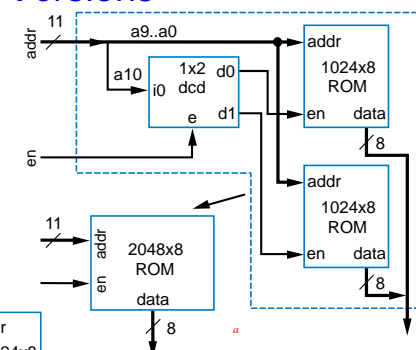 
## Hierarchy and Composing Larger Components from Smaller Versions

- Creating memory with more words
  - Put memories on top of one another until the number of desired words is achieved
  - Use decoder to select among the memories
    - Can use highest order address input(s) as decoder input
    - Although actually, any address line could be used
  - Example: Compose 1024x8 memories into 2048x8 memory



a10 just chooses which memory to access

To create memory with more words and wider words, can first compose to enough words, then widen.

88

## Chapter Summary

- Modern digital design involves creating processor-level components
- High-level state machines
- RTL design process
  - 1. Capture behavior: Use HLSM
  - 2. Convert to circuit
    - A. Create datapath B. Connect DP to controller C. Derive controller FSM
- More RTL design
  - More components, arrays, timers, control vs. data dominated
- Determining fastest clock frequency
  - By finding critical path
- Behavioral-level design – C to gates
  - By using method to convert C (subset) to high-level state machine
- Memory components (RAM, ROM)
- Queues
- Multiple processors
- Hierarchy: A key concept used throughout Chapters 2-5